# Conquering the Multi-Kilowatt Source/Sink Test Challenge



# Introduction

Satellites, hybrid electric vehicles (HEVs), electric vehicles (EVs), uninterruptable power supplies (UPSs), alternate energy power sources, and several other modern power systems supply power when it is opportune. They rely on bidirectional and regenerative energy systems and devices for storage to provide a continuous power supply on demand. Examples of these systems and devices include:

- Rechargeable batteries
- Supercapacitors
- Motor-generator systems
- Bidirectional DC/DC converters
- Battery management systems (BMS)
- Regenerative braking systems

Many of these systems and devices operate at multi-kilowatt power levels. When you develop and manufacture these systems, you need the ability to source and sink at kilowatt and greater power levels, which presents a formidable challenge for test engineers. The most common approach is to use separate instruments for sourcing and sinking because of their availability. However, this approach has shortcomings that can be overcome only by having the sourcing and sinking functions fully integrated into a single instrument or system.



# **Two-Quadrant Versus Four-Quadrant Operation**

Test engineers sometimes misunderstand what is needed for sourcing and sinking power for testing bidirectional and regenerative energy systems and devices. Bidirectional is often interpreted as bipolar, suggesting a bipolar power source is required for test purposes. These are two different things. A unipolar, bidirectional power source is one that operates in quadrants I and II of a four-quadrant I-V (current-voltage) plot, as shown in Figure 1. It can source and sink current but only with positive voltage. It operates as both a DC source and electronic load. It is a two-quadrant DC source.

A bipolar power supply can transition through zero volts and operate with either positive or negative voltage. It can source power in quadrants I and III and sink power in quadrants II and IV.

As these bidirectional and regenerative energy devices and systems source and sink current and have unipolar voltage, a unipolar two-quadrant DC source is almost always adequate and often preferable for testing them. It is important that the two-quadrant DC source has fully regulated continuous operation when used as an electronic load in quadrant II. Simple down programmer current sinking is insufficient for adequately testing these bidirectional energy systems and devices.


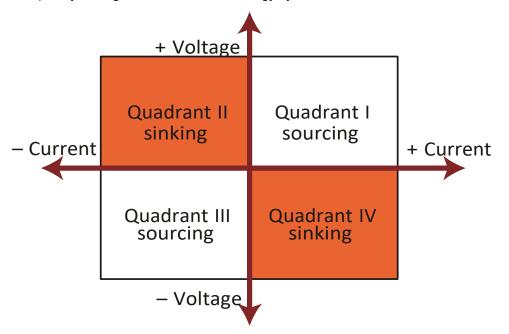


Figure 1. The four quadrants of an I-V plot
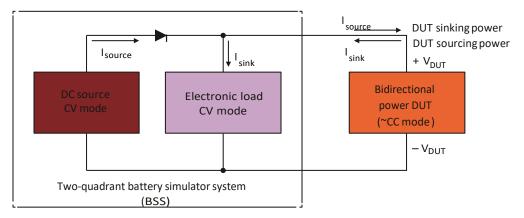
# Separate DC Source and Electronic Load with Deadband for Source-sink Operation

The selection of suitable two-quadrant DC sources at multi-kilowatt power levels is extremely limited. Engineers often use separate DC sources and electronic loads to provide the combined power sourcing and sinking needed for testing their bidirectional regenerative energy systems and devices. Independently, the DC source and electronic load are well suited for continuously sourcing and sinking power while providing good DC accuracy, stability, and fast dynamic response, regardless of the DUT. This kind of performance is needed, as these DUTs are active and dynamic, alternately sinking and sourcing power depending on their status and operating conditions.

One arrangement for combining a DC source and electronic load for source-sink operation is depicted in Figure 2, often used as a battery simulator system (BSS).



V e-load > (VDC source - Vdiode )

DUT sinking power, DC source active:  $V_{DUT} = (V_{DC \text{ source}} - V_{diode})$ 

DUT sourcing power, electronic load active: V<sub>DUT</sub> = V<sub>load</sub>

Figure 2. Common DC source and electronic load arrangement for a battery simulator system (BSS)

A BSS is predominantly a voltage device; both the DC source and the electronic load typically operate in constant voltage (CV) mode. Their voltage is offset to provide a deadband so that they do not overlap in operation, with the electronic load's voltage being set slightly greater than that of the DC source. Most often, the DUT being tested with a BSS is a battery management system (BMS), but this setup is applicable for various DUTs that need to be tested with a unipolar two-quadrant DC source. When the DUT is drawing or sinking power, the DC source maintains the voltage. When the DUT generates or sources power, the voltage rises, the DC source cuts off, and the electronic load becomes active, operating in CV mode, clamping the voltage at a slightly higher level. A blocking diode at the output of the DC source when the DUT is actively sourcing power. With this configuration, the source current is directly read back from the DC source, while the sink current is directly read back from the electronic load.



There are a number of performance compromises with this approach:

- The DC source needs to be used with local voltage sensing as the blocking diode will destabilize it if remote sensing around the diode is used.
- The deadband between sourcing and sinking is a high impedance.
- Voltage-level programming commands must be sent to both the DC source and electronic load to track each other as the BSS voltage level changes.
- Generally, a much higher level of complexity is needed to coordinate the DC source and electronic load activities during the test.
- The electronic load has to transition between cut-off and active CV mode, compromising its dynamic performance.
- The voltage drop of the blocking diode is variable based on current levels and temperature, leading to the need to use a substantial deadband voltage of a few hundred millivolts between the DC source and electronic load voltage levels.

These last two items limit this configuration's two-quadrant flexibility, accuracy, and general performance to static operation. To compensate for the deadband voltage under static operation, the BSS voltage can be programmatically brought up or down as needed to within a reasonably close voltage level. However, the deadband voltage step is inherent for dynamic transitions, further compounded by the electronic load's CV mode transient cross-over, as depicted in Figure 3.


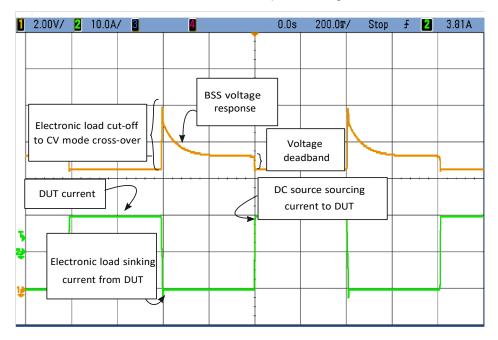


Figure 3. Source-sink transition for separate DC source and electronic load with deadband
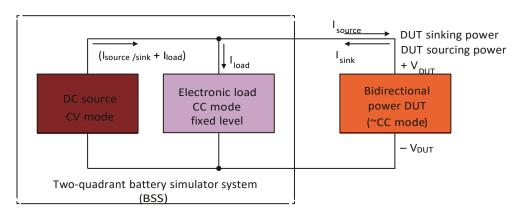
## Separate DC Source and Electronic Load with Overlapping Source-sink Operation

Fully overlapping operations can be used to avoid many of the problems associated with non-overlapping operations, as previously described. A DC source and electronic load configured for fully overlapping operation are depicted in Figure 4. Now, the electronic load operates in constant current (CC) mode instead of constant voltage (CV) mode. The electronic load's current setting is fixed at a value in excess of the maximum value expected to be sourced from the DUT. This way, the electronic load always remains in CC mode, drawing a fixed level of current and power. The electronic load no longer has to contend with any mode cross-over issues. The DC source always remains in CV mode and is constantly sourcing current. Because of this, the blocking diode is no longer required. As a result, this BSS configuration is always in CV mode throughout the entire range of sourcing and sinking, free of the electronic load mode cross-over and the deadband voltage transients affecting the BSS configuration that has non-overlapping operation. There are a few drawbacks as a result:

- The DC source needs to be considerably larger to furnish both the maximum current and power required by the DUT plus the full amount that the electronic load continually draws. For example, the DC source must be more than twice as large for 100% current sinking.
- The electronic load constantly dissipates full power, which is considerable for a large system.
- Measurements require reading back both the DC source and electronic load currents and taking the difference, often of two large values to get one small value. Measurement accuracy suffers as a result.



ILoad > (I sink-max), fixed value

VDUT = VDC source

DUT sinking power: IDC source = (Isource + Iload)

DUT sourcing power: IDC source = (Isink (negative) + Iload)

Figure 4. DC source and electronic load with overlapped operation for a battery simulator system (BSS)



## **Integrated Source-sink Solutions**

The disadvantages of configuring a power sourcing and sinking solution with a separate DC source and electronic load are mitigated when the sourcing and sinking functions are integrated into a single instrument. When integrated, these functions operate under closed-loop control to provide seamless, transient-free cross-over between sourcing and sinking current and power. There is no need to constantly dissipate large amounts of power to accomplish this. DC accuracy and dynamic performance are now optimized instead of compromised. Measurement performance is greatly improved by having a single measurement system for all currents. The main challenge has been a lack of instruments that adequately address the test needs of today's bidirectional and regenerative energy systems and devices, and it leaves engineers no choice but to use separate DC sources and electronic loads.

## Keysight Advanced Power System (APS) N6900/N7900/RP7900 DC Power Supplies Featuring Integrated Sourcing and Sinking

#### **Key features**

The APS N6900A/N7900A/RP7900 DC power supplies, pictured in Figure 5, are tailored for the test needs of today's bidirectional and regenerative energy systems and devices. Notable features include:

- Energy efficient 1U-tall, 1-kW models, 2U-tall, 2-kW models, 3 U-tall, 5 to 20KW models, and 5U-tall, 30-KW models provide high power in minimum space.
- 10% current and power sinking integrated capability is built in for N6900A/N7900A models. Easily increased to up to 100% sinking with the optional N7909A Power Dissipator Unit.
- 100% continuous sinking integrated capability is built in for RP7900 models without needing an external power dissipation unit.
- A wide selection of output voltages addresses the diversity of today's DUTs and applications.
- Voltage- and current-priority operation give greater sourcing and sinking test flexibility, regardless of the DUT's nature.
- Two-quadrant measurement system for accurate voltage, current, power, charge, and energy measurements.
- Advanced sourcing and measurement capabilities in the APS N7900/RP7900 models can create dynamic output events, make transient measurements, continuously log voltage, current, power, and more.
- Advanced trigger signal routing with configurable logic for creating application-specific controls, triggers, and protection features, useful for easily solving particularly challenging test problems.
- Unique modular architecture for easily scaling integrated source-sink systems of up to 30-kW for testing higher-power DUTs.



#### **Physical appearance**



1-kW power sourcing in 1U

1-kW power dissipation in 1U

2-kW power sourcing in 2U

20-kW power sourcing and dissipation in 3U

	10
HYSER PYECA PYECA BYTECA B	It "
	J.

Figure 5. Keysight APS N6900/N7900/RP7900 models

30-kW power sourcing and dissipation in 5U



### **Key specifications**

#### Table 1. Keysight APS N6900/N7900 models

	APS N6900A DC Power Supply		APS N7900A Dynamic DC Power Supply	
	1000 W	2000 W	1000 W	2000 W
9 V	100 A (900W)	200 A (1800 W)	100 A (900 W)	200 A (1800W)
20 V	50 A	100 A	50 A	100 A
40 V	25 A	50 A	25 A	50 A
60 V	17 A	33 A	17 A	33 A
80 V	12.5 A	25 A	12.5 A	25 A
120V	Not Applicable	16.7A	Not Applicable	16.7A
160V	Not Applicable	12.5A	Not Applicable	12.5A

#### Table 2. Keysight RP7900 models

#### **RP7900 Series Regenerative Power System**

	5kW	10kW
20V	400A	800A
80V	125A	250A
160V	Not Applicable	125A
500V	20A	40A
950V	Not Applicable	20A

#### **RP7900 Series Regenerative Power System**

	20kW	30kW
1000V	60A	90A
1500V	Not Applicable	60A
2000V	30A	30A



# APS integrated sourcing and sinking for seamless operation

When you use separate DC sources and electronic loads, you don't have access to built-in power sinking. The N6900 series and N7900 series APS units feature 10% power sinking built-in. They can be effortlessly increased up to 100% integrated sinking capability by simply adding one or two 1-kW N7909A Power Dissipator Units, depending on the APS unit's power rating. All that is required is to connect a power cable and a control cable between the two units to provide truly integrated operation, as shown in Figure 6. As you can see in Figure 7, even with 10X greater voltage resolution, an APS and N7909A provide seamless, stable voltage performance while transitioning between sourcing and sinking when tested under conditions comparable to the separate DC source and electronic load BSS setup shown in Figures 2 and 3.

As for the RP7900 series, it sinks up to 100% directly of its rated current for an indefinite time continuously without a power dissipation unit. The RP7900 also can provide seamless source-sink transition, as depicted in Figure 8.

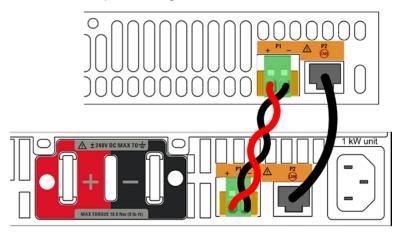


Figure 6. Integrating an APS N6900/N7900 model and an N7909A power dissipator unit

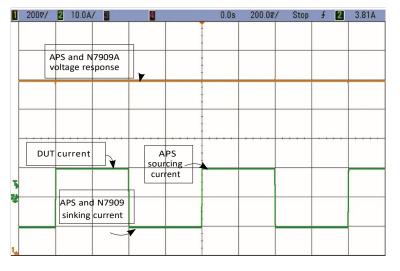


Figure 7. APS N6900/N7900 and N7909A seamless source-sink response



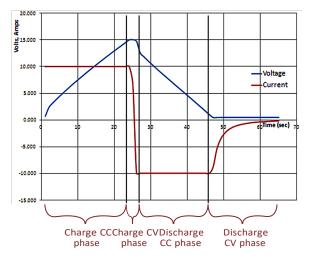



Figure 8. RP7900 series source-sink response

#### **APS advanced measurement performance**

Making accurate voltage, current, power, charge, and energy measurements is necessary to test bidirectional and regenerative energy systems and devices. These measurements are complicated and problematic when you use a separate DC source and electronic load as a basis for a source-sink test solution. At a minimum, separate currents read back from the DC source, and the electronic load must be managed and assimilated. In all likelihood, the DC source and electronic load will not have adequate capabilities for making accumulated charge and energy measurements, requiring you to add external logging measurement capability with its associated complexity and issues.

The APS's integrated two-quadrant measurement system fully complements its sourcing and sinking capability. Making accurate voltage, current, power, charge, and energy measurements is straightforward when using an APS. As one example, Figures 9 and 10 depict the current, voltage, and energy sourced and then subsequently recovered on a supercapacitor when using an APS and N7909A Power Dissipator Unit for charging and discharging the supercapacitor while capturing its voltage, current, and energy.



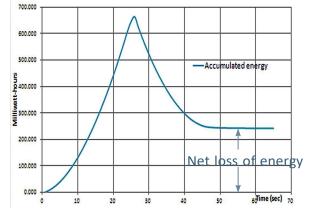

**Figure 9.** Supercapacitor charging and discharging voltage and current

**Figure 10.** Supercapacitor charging and discharging energy



# Summary

Satellites, hybrid electric vehicles (HEVs), electric vehicles (EVs), uninterruptable power supplies (UPSs), alternate energy power sources, and several other modern power systems rely on bidirectional and regenerative energy systems and devices. Many of these bidirectional energy systems and devices operate at multi-kilowatt power levels. Accordingly, the development and manufacturing of these systems and devices dictate having the ability to source and sink at kilowatt and greater power levels, which is a formidable challenge for test engineers.

The most common approach is to use a separate DC source and electronic load for sourcing and sinking. However, this leads to several issues and compromises because the sourcing and sinking are independent. They can provide optimum, seamless performance only when sourcing and sinking are truly integrated into a single system.

The Keysight Technologies APS N6900/N7900/RP7900 DC power supplies feature integrated sourcing and sinking capability tailored for the test needs of today's bidirectional and regenerative energy systems and devices. As a result, the Keysight APS N6900/N7900/RP7900 DC power supplies overcome all the challenges of creating a high-power source-sink test solution, providing optimum performance that only an integrated solution can do, freeing up test resources to tackle other challenges needing conquering!

#### For more information

N6900 Series Advanced Power Supplies, visit www.keysight.com/find/N6900 N7900 Series Advanced Power Supplies, visit www.keysight.com/find/N7900 RP7900 Series Regenerative Power Supplies, visit www.keysight.com/find/RP7900

Keysight enables innovators to push the boundaries of engineering by quickly solving design, emulation, and test challenges to create the best product experiences. Start your innovation journey at www.keysight.com.



This information is subject to change without notice. © Keysight Technologies, 2018 – 2023, Published in USA, October 3, 2023, 5991-2873EN